

LAB 6: MULTIPLEXERS AND STATE MACHINE

1.0 Objectives

- Designing, implementing and testing a three-bit wide 5-to-1 multiplexer and a finite state machine for a sequence counter using Verilog entry.

2.0 Results and Simulation

A. Multiplexer

```
module fivemux (S, U, V, W, X, Y, M);  
    input [2:0] S;  
    input U, V, W, X, Y;  
    reg M;  
    output M;  
    //output [2:0] M;  
    //reg [2:0] M;  
    always@(U or V or W or X or Y or S or M)  
        if (S == 3'b000)  
            M = U;  
        else if (S == 3'b001)  
            M = V;  
        else if (S == 3'b010)  
            M = W;  
        else if (S == 3'b011)  
            M = X;  
        else if (S == 3'b100)  
            M = Y;  
        else M = 0;  
endmodule
```

Figure 1: 5-to-1 Multiplexer Code

Table 1: Truth table obtained from 5-to-1 multiplexer

SELECT LINES			INPUTS					OUTPUT
S2 [SW2]	S1 [SW1]	S0 [SW0]	U [SW4]	V [SW5]	W [SW6]	X [SW7]	Y [SW8]	M [LED0]
0	0	0	1	0	0	0	0	1
0	0	1	0	1	0	0	0	1
0	1	0	0	0	1	0	0	1
0	1	1	0	0	0	1	0	1
1	0	0	0	0	0	0	1	1

	tatu	From	To	Assignment Name	Value	Enabled	Entity	Comment	Tag
1	✓		in S[1]	Location	PIN_AC12	Yes			
2	✓		in S[2]	Location	PIN_AF9	Yes			
3	✓		out M	Location	PIN_V16	Yes			
4	✓		in U	Location	PIN_AD11	Yes			
5	✓		in V	Location	PIN_AD12	Yes			
6	✓		in W	Location	PIN_AE11	Yes			
7	✓		in X	Location	PIN_AC9	Yes			
8	✓		in Y	Location	PIN_AD10	Yes			
9	✓		in S[0]	Location	PIN_AB12	Yes			

Figure 2: 5-to-1 Multiplexer Pin Assignments

 


Figure 3: 5-to-1 Multiplexer in Operation on Board

B. Finite State Machine

```
module fsm_counter (clk, reset, outp);
    input clk, reset;
    output [2:0] outp; //reg [2:0] outp;

    wire [2:0] outp;
    reg [2:0] c_state;

    //define all possible state
    parameter s1 = 3'b000; parameter s2 = 3'b110;
    parameter s3 = 3'b111; parameter s4 = 3'b011;
    parameter s5 = 3'b010; parameter s6 = 3'b101;

    //your code here

    initial
    begin
        c_state = s1;
    end

    always@(posedge clk, posedge reset)
    begin
        if(reset) //Set Counter to Zero
            c_state <= s1;
        else if(c_state == 3'b000)
            c_state = s2;
        else if(c_state == 3'b110)
            c_state <= s3;
        else if(c_state == 3'b111)
            c_state <= s4;
        else if(c_state == 3'b011)
            c_state <= s5;
        else if(c_state == 3'b010)
            c_state <= s6;
        else
            c_state <= 3'b000;
    end

    assign outp = c_state;
endmodule
```

Figure 4: Finite State Machine Counter Code

	tatu	From	To	Assignment Name	Value	Enabled	Entity	Comment	Tag
1	✓		in S[1]	Location	PIN_AC12	Yes			
2	✓		in S[2]	Location	PIN_AF9	Yes			
3	✓		out M	Location	PIN_V16	Yes			
4	✓		in U	Location	PIN_AD11	Yes			
5	✓		in V	Location	PIN_AD12	Yes			
6	✓		in W	Location	PIN_AE11	Yes			
7	✓		in X	Location	PIN_AC9	Yes			
8	✓		in Y	Location	PIN_AD10	Yes			
9	✓		in S[0]	Location	PIN_AB12	Yes			

Figure 5: Finite State Machine Counter Pin Assignment

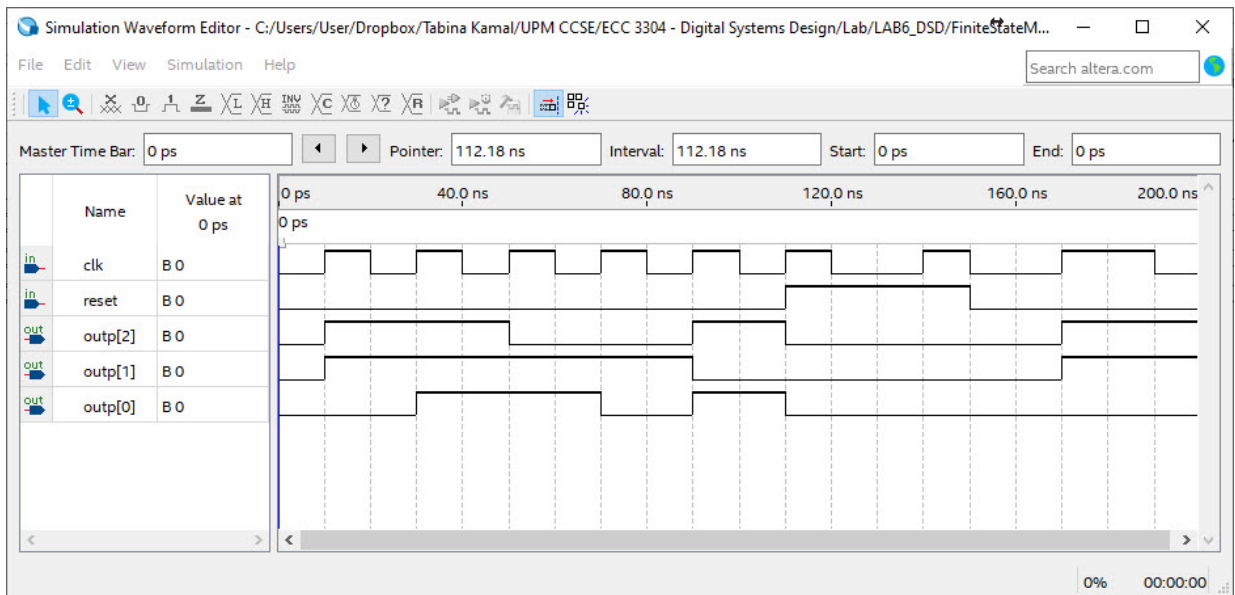


Figure 6: Finite State Machine Counter Functional Simulation

 


Figure 7: State Diagram

3.0 Conclusion

A. Multiplexer

Successfully compiled and demonstrated.

B. Finite State Machine

Successfully compiled and simulated.

Not yet implemented on the board.